

1 Introduction

In this lab, we examine the voltage transfer characteristics of the current-mirror differential amplifier and its output-voltage range. We then compute the differential mode-voltage gain in two different ways. Finally, we investigate the time response of the amplifier configured as a unity-gain follower to both small-amplitude and large-amplitude steps. The circuits are constructed using ALD1106 quad nMOS and ALD1107 quad pMOS transistor arrays, and a source-measurement unit (SMU) was used to supply and measure voltage and current.

2 Experiment 1: Voltage Transfer Characteristics

In this experiment, we constructed a current-mirror differential amplifier with an nMOS differential pair, two simple pMOS current mirror, and a simple nMOS current mirror. We set three values of the inverting input, $V_2 = 2V, 3V, 4V$. For each value of V_2 , we swept the noninverting input, V_1 , from rail to rail and measure the output, V_{out} . As seen in Figure 1, $V_{out} = 0$ when $V_1 < V_2$, and $V_{out} = 5V$ when $V_1 > V_2$. This is different from the amplifier we looked at in Lab 8 under the condition $V_1 < V_2$. In Lab 8, we saw V_{out} increase up to the point where $V_1 = V_2$, while in this lab, it appears that V_{out} remains at zero up until that point.

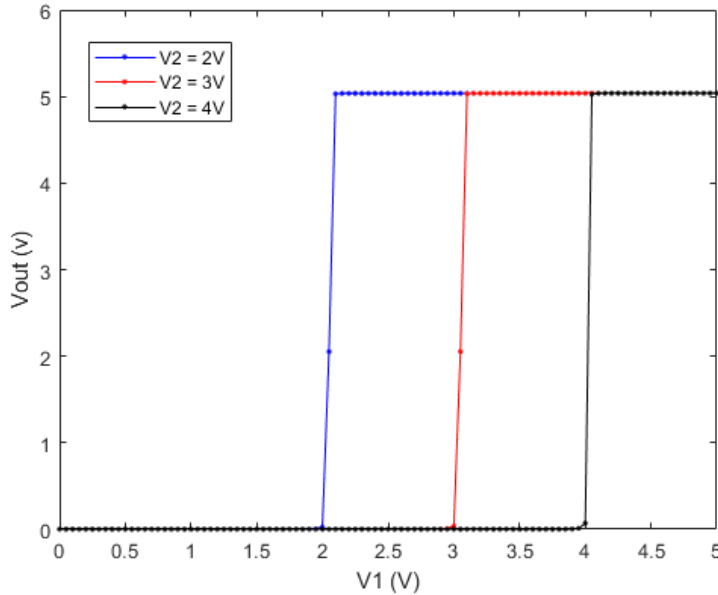


Figure 1: V_{out} vs. V_1 for three values of V_2 with $V_b = 0.65V$

3 Experiment 2: Transconductance, Output Resistance, and Gain

In this experiment, we started with the same circuit as Experiment 1 and set $V_2 = 3V$ and measured V_{out} , but instead of sweeping V_1 from rail to rail, we swept it around V_2 in fine increments. As seen in Figure 2, the linear fit matches the steep part of our voltage transfer characteristic. The slope of the linear fit is the differential-mode gain, A_{dm} , of the amplifier, where $A_{dm}=234.2$.

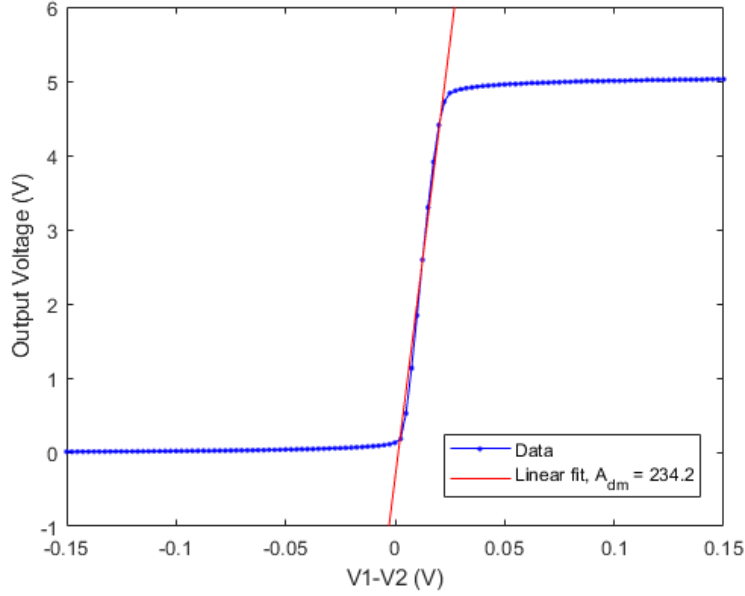


Figure 2: V_{out} vs. $V_1 - V_2$ for fixed $V_2 = 3$, $V_b = 8V$

Next, we set the differential-mode input voltage, V_{dm} , to zero, and swept V_{out} from one rail to the other while we measured the current out, I_{out} , of the amplifier. The linear fit displayed in Figure 4 matches the data where the amplifier's gain is large. The slope of this fit allows us to find the incremental output resistance, $R_{out} = 4.06e+06 \Omega$.

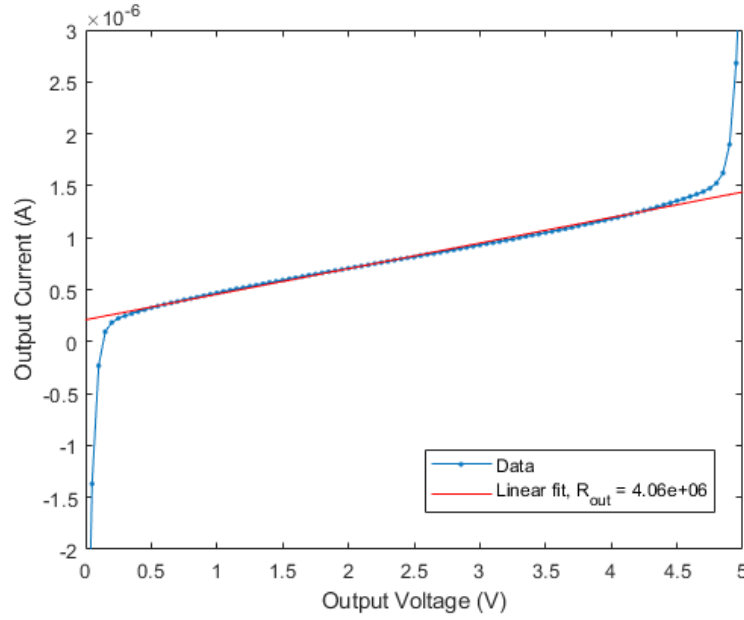


Figure 3: I_{out} vs. V_{out} when $V_{dm} = 0$, $V_b = .8V$

Finally, we fixed $V_{out} = 3V$, swept V_{dm} around zero, and measured I_{out} . The slope of the linear fit in Figure 4 gives us the incremental transconductance gain, $G_m = 5.96e-05$ Mhos.

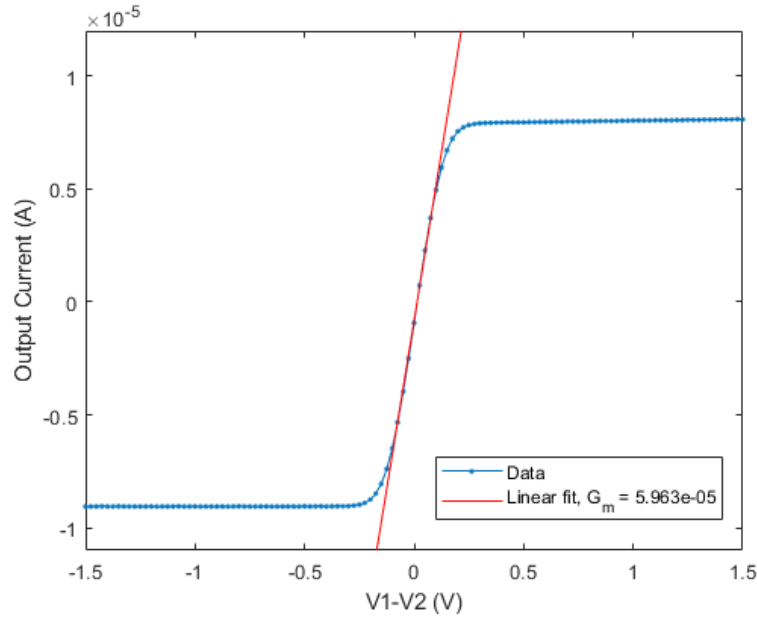


Figure 4: I_{out} vs. $V_1 - V_2$ when $V_{out} = 3$, $V_b = .8V$

From the equation, $A_{dm} = R_{out} * G_m = 242.3$. This is very close to the value $A_{dm} = 234.2$ that we got from the slope of the VTC. The differential-mode gain of this amplifier is also close to the one we investigated in Lab 8, where we found that $A_{dm} = 260.47$.

4 Experiment 3: Unity-Gain Follower

In this experiment, we configured the amplifier as a unity-gain follower by connecting V_{out} to V_2 . We then added a $1nF$ pull-down capacitor between the output of the amplifier and ground. We applied a small-amplitude square wave of $.1V$ to the input of the circuit and observed both the input and output waveforms as a function of time. The DC offset was set to $3V$.

The response is symmetrical, as seen in Figure 5. The amplifier does not exhibit linear behavior.

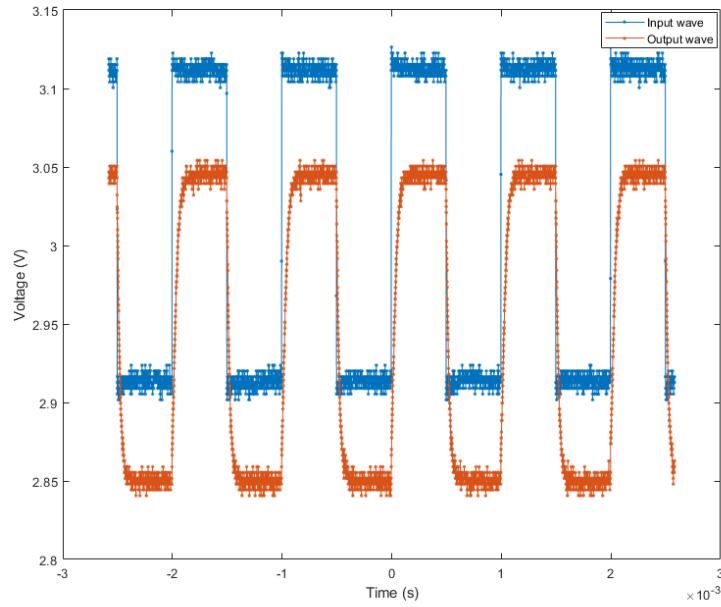


Figure 5: Input and Output Voltages with a small-amplitude square wave of $.1V$

We then increased the amplitude of our square wave so that it has an amplitude of $1.5V$. The response was not symmetrical, as seen in Figure 6. The slew rate for the up-going part is $2.8388e+03$ V/s, while for the down-going part it is $-6.9521e+03$ V/s.

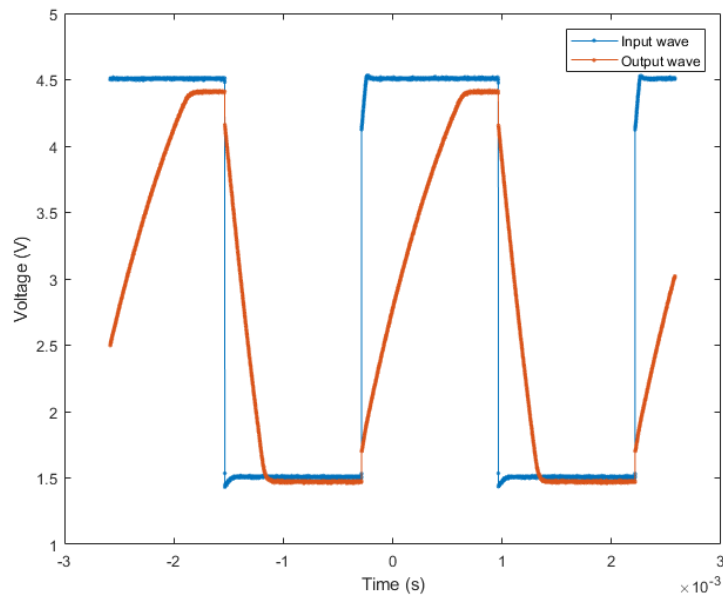


Figure 6: Input and Output Voltages with a large-amplitude square wave of 1.5V